

Single-phase PV inverter with Fictive-Axis Emulation

AN003 | Posted on March 30, 2021 | Updated on July 24, 2025



Gabriel FERNANDEZ
Operations Manager
imperix • in




Nicolas CHERIX
Head of Engineering
imperix • in

Table of Contents

- [Downloads](#)
- [Single-phase PV inverter control implementation](#)
 - [Grid-side control](#)
 - [PV-side control](#)
- [Simulation results of single-phase PV inverter](#)
- [Useful academic references](#)
- [Physical realization of the single-phase PV inverter](#)
 - [Required hardware](#)
 - [I/O signals](#)
 - [Start-up procedure](#)


This application note presents a possible control implementation for a single-phase PV inverter, controlling the grid current in the dq reference frame. This approach requires the emulation of quadrature components that do not exist in a single-phase system, hence justifying the use of a dedicated emulation principle named fictive-axis emulation. The attractiveness of this approach is related to its excellent capability to decouple the control of the active and reactive power flows.

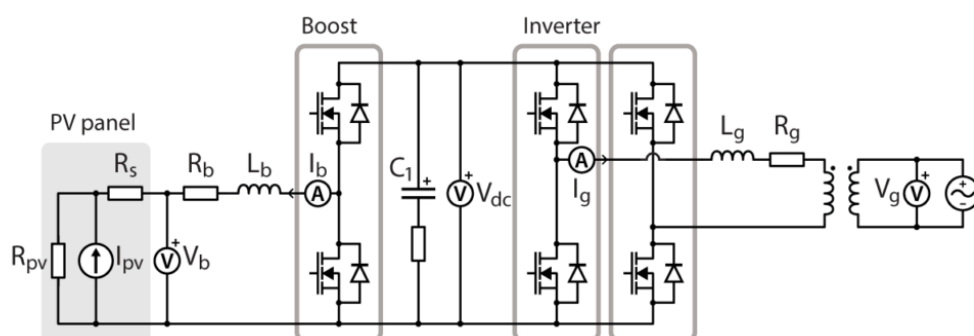

Downloads

The following zip file contains an example of control using [MATLAB Simulink](#).

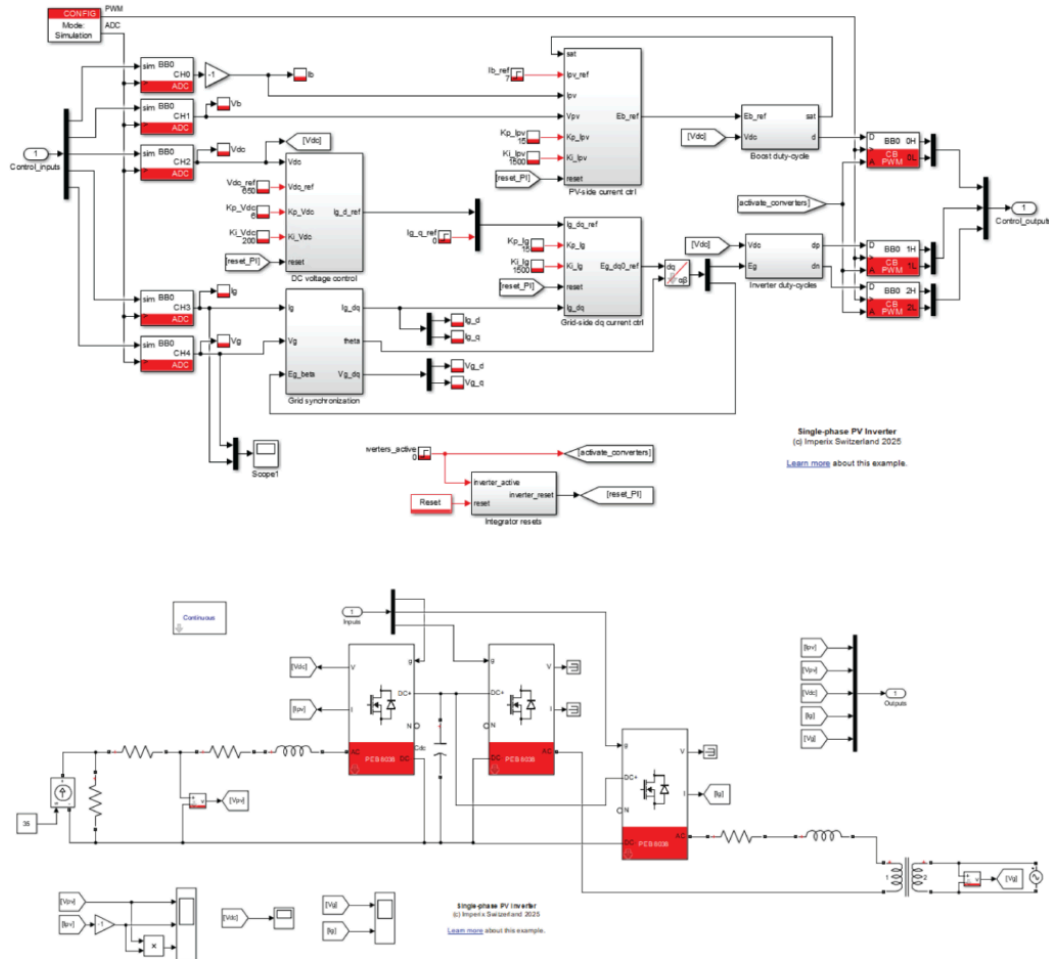[AN003_single_phase_PV_inverter_SimulinkDownload](#)



Minimum requirements:

- Imperix ACG SDK 3.5.1.1 or newer.
- MATLAB Simulink R2016a or newer.

Single-phase PV inverter control implementation

The proposed control is implemented on MATLAB Simulink using the associated blockset for [B-Box RCP](#) / [B-Board PRO](#) (part of imperix [ACG SDK](#)). The chosen control implementation consists in controlling the grid current using a rotating reference frame (dq-type) synchronized with the grid frequency. The attractiveness of this approach is related to its excellent capability to decouple the control of the active and reactive power flows. Additionally, the mechanisms commonly used in three-phase applications can be re-used directly. On the other hand, this approach

Alternatively, the grid current could also be controlled using a Proportional Resonant (PR) controller [Proportional Resonant \(PR\) control \(TN110\)](#), which would circumvent the need for FAE, but at the cost of a less intuitive decoupling of active and reactive power flows.


Grid-side control

The grid current itself is controlled thanks to a conventional dq-based vector current control, which is further detailed in [Vector current control \(TN106\)](#). As such, the reactive power flow can be freely defined through $I_{g\beta}$, while the active power flow is controlled through $I_{g\alpha}$ by the bus voltage controller.

The diagram illustrates the control system for a converter. It starts with input voltages V_g (2) and V_{dc} (3). V_g is processed by a SOGI-PLL block to produce $V_{g\alpha}$, $V_{g\beta}$, and θ . V_{dc} is used for DC voltage control, which outputs U_{dc} and I_{d_ref} . I_{d_ref} is then multiplied by -1 to produce $I_{g_q_ref}$. The FAE block takes V_{g_be} and I_{g_be} as inputs and outputs I_g (1). The DQ current control block takes $I_{g_q_ref}$ and I_g as inputs and outputs I_{g_dqref} and I_{g_dq} . The $\alpha\beta$ to dq transformation block takes I_{g_dq} and θ as inputs and outputs dq and $\alpha\beta$. The dq to $\alpha\beta$ transformation block takes dq and $\alpha\beta$ as inputs and outputs E_g (1). The text box explains that the -1 sign is due to the fact that the grid current is positive when flowing out of the converter.

The DC bus voltage control implements a conventional cascaded PI controller [Cascaded voltage control \(TN108\)](#), but with the particularity that a notch filter is placed on the error input in order to remove double-frequency components (here

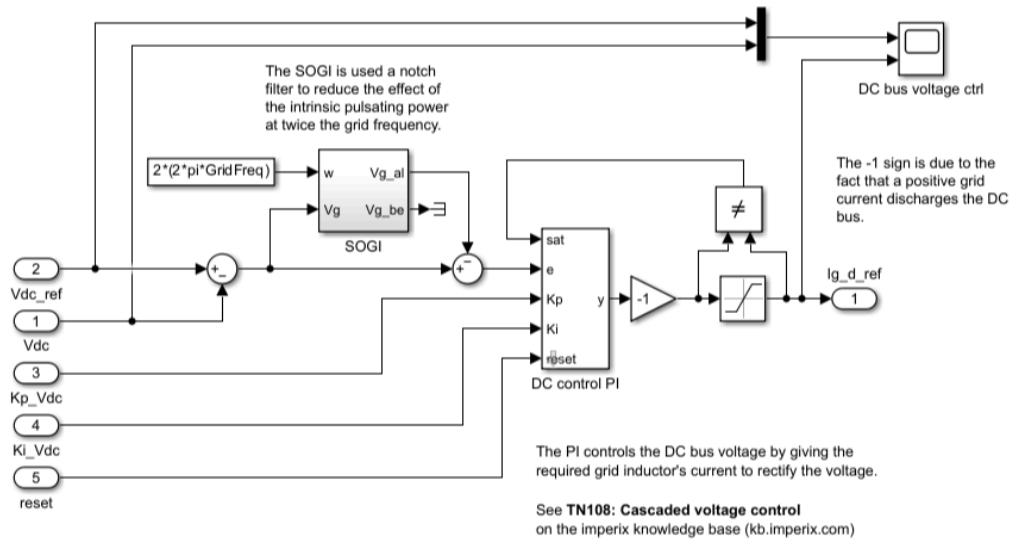100Hz) from the controller output $I_{g,d}$. Indeed, single-phase systems intrinsically have pulsating instantaneous active power flows, which results in DC voltage oscillations. These oscillations are therefore desirable *by design* and shall not be rejected by the voltage controller.





PV-side control

The PV current is controlled thanks to a conventional PI controller, whose reference can be freely defined. No Maximum Power Point Tracking (MPPT) is implemented in this example. This topic is nevertheless addressed in [Maximum Power Point Tracking \(MPPT\) \(TN117\)](#).

Simulation results of single-phase PV inverter

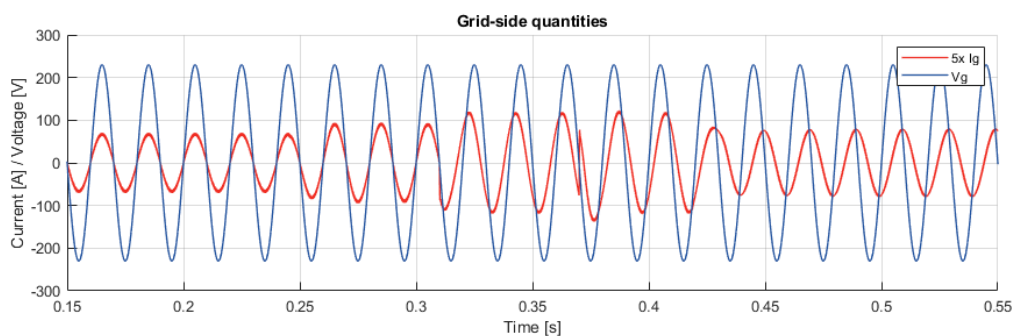Simulation results are provided below, showing various transients due to active and reactive power setpoint changes. Notably, the reference steps on the PV current (I_b) indirectly impacts the d-axis grid current ($I_{g,d}$), through the DC bus voltage control.



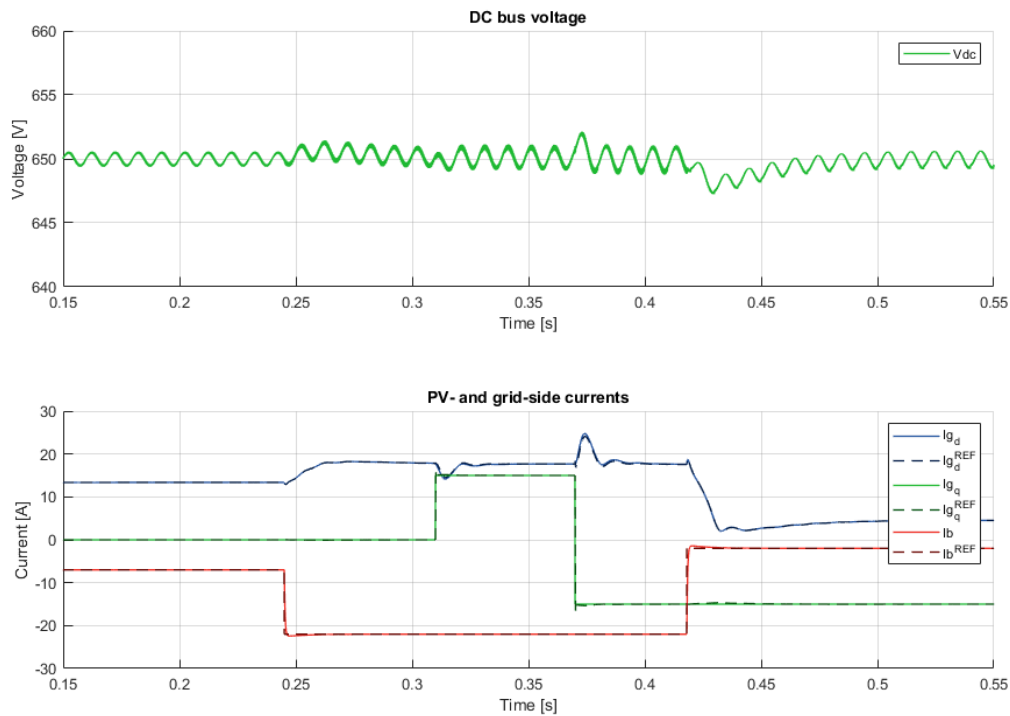

Useful academic references

- [1] B. Bahrani, S. Kenzelmann and A. Rufer, "Multivariable-PI-based dq current control of voltage source converters with superior axis decoupling capability," in IEEE Trans. Ind. Electron., Vol. 58, N° 7, Jul. 2011.
- [2] M. Ciobotaru, R. Teodorescu and F. Blaabjerg, "A new single-phase PLL structure based on a second-order generalized integrator," in Proc. PESC Conf., Rhodes, Greece, June 2006.
- [3] F.J. Rodríguez, E. Bueno, M. Aredes, L.G.B. Rolim, F.A.S. Neves and M.C. Cavalcanti, "Discrete-time implementation of second-order generalized integrators for grid converters," in Proc. IECON Conference, Orlando, Nov. 2008.
- [4] R. Teodorescu, F. Blaabjerg, M. Liserre, and P. C. Loh, "Proportional resonant controllers and filters for grid-connected voltage-source converters," in IEE Proc. on Electr. Power Appl., Vol. 153, N°. 5, Sep. 2006.

Physical realization of the single-phase PV inverter

An obvious prerequisite of grid-tied operation is that all necessary precautions are used in order to **make the flow of uncontrolled currents through the inverter diodes impossible**. This notably requires that the DC bus is pre-charged by suitable means

before the connection to the grid. Useful information regarding how to pre-charge the DC bus in grid-tied applications is given in [TN131](#).

Don't forget to properly configure protection thresholds on the B-Box RCP **before starting** experimental activities. The related documentation can be found in [PN105](#).


Required hardware

Experimentation on this Application Note can be made using standard imperix equipment:

- 1x "Type C" rack with 3x [PEB8024](#) modules
- 1x [passive filters](#) rack or:
 - 1x 2.5mH inductor (L_g)
 - 1x 5.0 mH inductor (L_b)
- 2x [DIN800V](#) voltage sensors

In addition, the following equipment is needed:

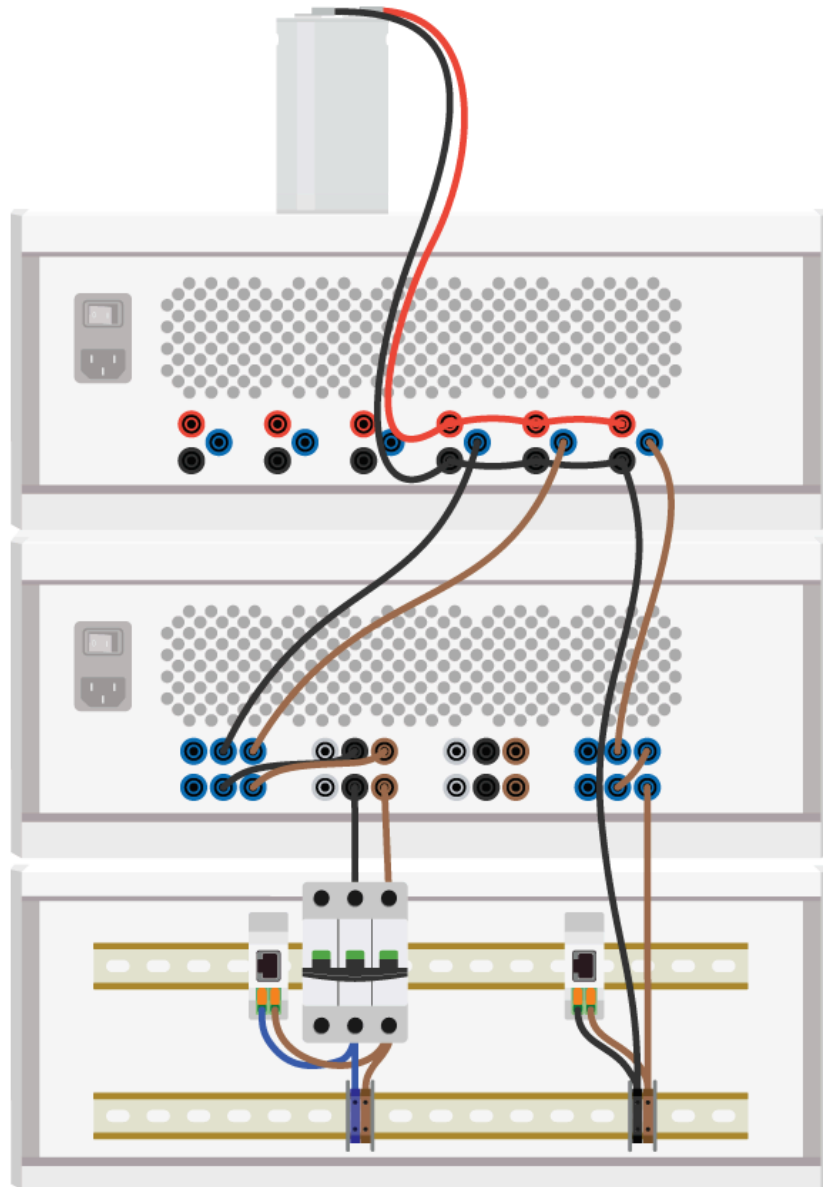- 1x 7.5mF DC bus capacitor (C_{dc})
- 1x PV panel or PV panel emulator
- 1x isolation transformer (not shown)
- 1x AC disconnect, or better controllable relay as well as a circuit breaker.
- (1x pre-charge circuit – optional, not shown)



I/O signals

Controller inputs (sensors)

- AIN0 – PV current (I_b) – [PEB8024](#)
- AIN1 – PV voltage (V_b) – [DIN800V](#)
- AIN2 – DC voltage (V_{dc}) – [PEB8024](#)
- AIN3 – AC current (I_g) – [PEB8024](#)
- AIN4 – AC voltage (V_g) – [DIN800V](#)

Controller outputs (PWM signals)

- *PWM0-PWM1* – Boost converter
- *PWM2-PWM3* – Grid inverter, leg A
- *PWM4-PWM5* – Grid inverter, leg B

PWM0 can most often be avoided unless reverse conduction in the MOSFET is desired.

Start-up procedure

The following steps can be used as a brief reminder of a reasonable start-up procedure:

1) Before addressing this application, run a simpler control code in order to validate that:

- ✓ All measurements are correctly acquired, with the appropriate gain and sign (notably currents).
- ✓ Protections are correctly configured and do trigger at the appropriate value.
- ✓ The switched voltage (EMF) at the converter-side of the grid inductor has no obvious phase mismatch with the grid voltage (e.g. operating in open-loop while disconnecting the inductor). There are indeed numerous risks of polarity errors...

2) Pre-charge the DC bus to a sufficient voltage to avoid any risk of uncontrolled diode conduction. In single-phase application, the minimum DC bus voltage is defined by $V_{DC,min} = \widehat{V}_g$. Check [DC bus pre-charging techniques](#) for more details.

Double-check this condition.

3) Physically connect the converter to the grid, either using a controllable relay or using manual wiring.

4) In Cockpit, enable PWM operation. Related getting-started instructions are available in [Programming and operating imperix controllers \(PN138\)](#).