

SVPWM vs SPWM modulation techniques

TN146 | Posted on August 19, 2021 | Updated on May 7, 2025



Simon STROBL

Product Director

imperix • in

Table of Contents

- [What are SVPWM and SPWM?](#)
 - [Limitation of the DC bus utilization with SPWM](#)
 - [Min/max injection with SVPWM](#)
- [Experimental comparison](#)
 - [Simulink implementation](#)
 - [SVPWM and SPWM waveforms](#)
- [Academic references](#)

What is the difference between Space Vector (SVPWM) and Sinusoidal Pulse Width Modulation (SPWM)? This article presents the advantages of the SVPWM technique over SPWM in the case of a two-level three-phase inverter.


A demonstration code example is provided and freely available. It can be tested in simulation using imperix [ACG SDK](#) and validated in the laboratory with a [B-Box RCP](#) programmable controller and [PEB half-bridge power modules](#).



What are SVPWM and SPWM?

SVPWM and SPWM are two modulation techniques commonly used with power converters. The purpose of a modulation scheme is to translate a voltage reference into a sequence of switching signals, in order to produce that reference at the output of the converter. While both techniques share similar acronyms, they have fairly different approaches.


On one hand, the [SVPWM technique](#) represents each switching state of the converter by a space vector in the [Clarke referential](#). Then, the desired output voltage is synthesized on average, by alternating between multiple space vectors over each switching period. On the other hand, SPWM is a Carrier-Based PWM scheme ([CB-PWM](#)) with a sinusoidal reference (see the note on the [voltage source inverter](#)). In order to simplify the comparison, only the case of two-level three-phase inverters is covered. The topology of the inverter is shown in the figure below.

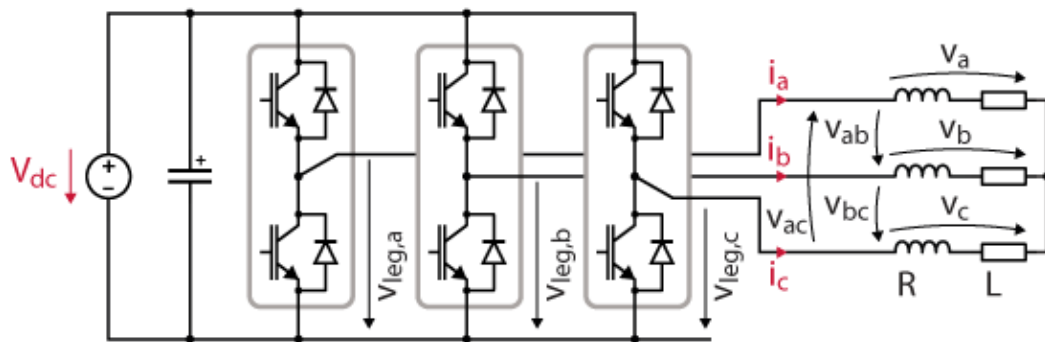

Topology of a two-level inverter with an RL load

Limitation of the DC bus utilization with SPWM

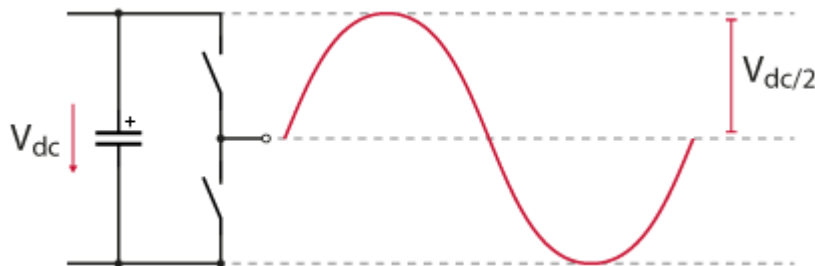While producing a sinusoidal phase voltage with a two-level inverter, the peak amplitude is limited by the DC bus voltage [1]. Based on the illustration below, each leg of the inverter can produce a leg voltage v_{leg} of amplitude $V_{DC}/2$.




Limitation of the output phase voltage by the DC bus

The relative amplitude of the output voltage is often referred to as the *modulation index*, denoted m [1], and the maximum amplitude of the sinusoidal voltage

corresponds to $m = 1$. Thus, the phase voltage can be expressed as a function of the modulation index m , the angular frequency ω , and the phase ϕ :

$$v_{phase}(t) = m \frac{V_{DC}}{2} \sin(\omega t + \phi)$$

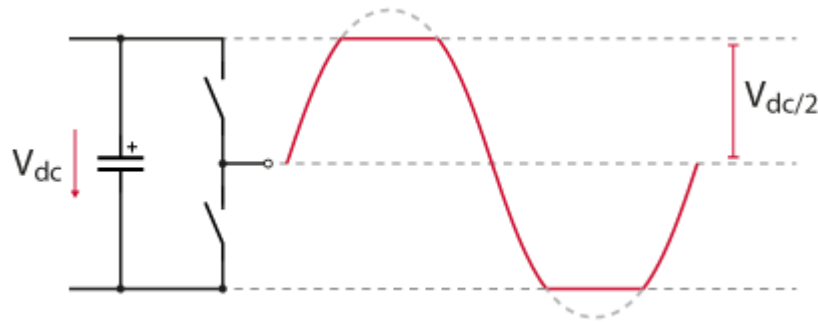
If $m > 1$, the output voltage will be clipped to $\pm V_{DC}/2$. As such, the distortion introduces low-order harmonics that can be difficult to filter out. If the voltage reference exceeds the DC bus capabilities, the converter is said to be in the overmodulation region.



Clamping of the output voltage in the overmodulation region

Min/max injection with SVPWM


It can be demonstrated that SVPWM is equivalent to an SPWM with min/max injection [1]. The idea behind the min/max injection method is to add a triangular zero sequence component (triplen harmonics) to the sinusoidal reference, which distorts the phase voltage references. This way, the peak voltage of the reference is reduced in comparison to a pure sinusoidal reference, and the modulation index can be increased up to $m = 2/\sqrt{3} \approx 1.15$ before hitting the limits of the DC bus voltage.

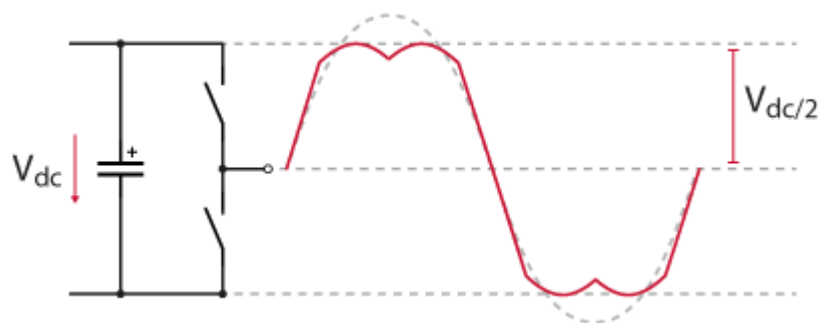

Reduction of the peak output voltage with min/max injection

If the inverter is connected to a load with a grounded star connection, the distortion of the phase voltages is propagated to the line-to-line voltages, as shown below in Fig. (a). As a result, the load currents are also distorted, and SVPWM is not a suitable modulation scheme in terms of harmonic content. Fortunately, it is possible to suppress the distortions in the line-to-line voltages by using different wiring of the

load. If the star connection is floating – see Fig. (b) – the triplen harmonics of the zero-sequence will cancel each other out, and the line-to-line voltages remain unaffected. The situation is similar in the case of a delta-connected load – see Fig. (c) – since the phase voltages of the load are equal to the line-to-line voltages produced by the inverter. Thus, for delta or floating star connections, SVPWM allows increasing the maximum line-to-line voltage without distortion of the load currents.

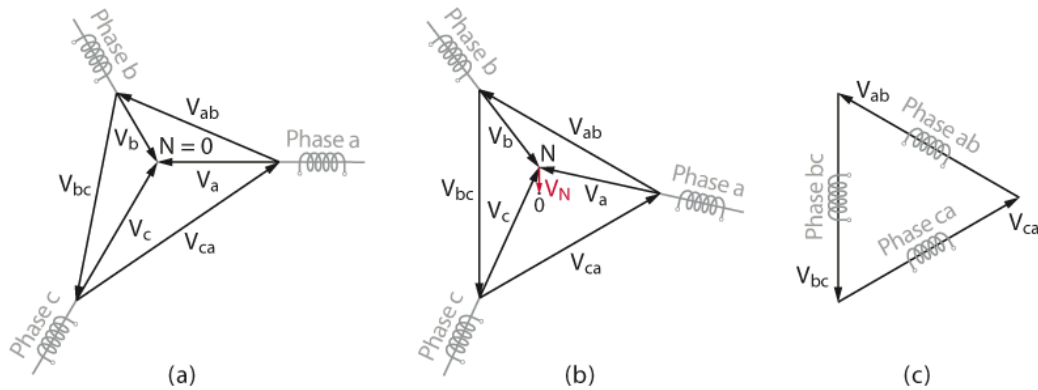


(a) Distortion of the line-to-line voltages when the star is grounded; (b) the triplen harmonics cancel each other out when the star is floating; (c) no triplen harmonics neither with a delta connection.

Experimental comparison

Simulink implementation


The model provided in this article executes a simple open-loop voltage control of a two-level three-phase inverter. For comparison purposes, both SVPWM and SPWM (with or without min/max injection) techniques are implemented in parallel, and the user can select which switching signals will drive the converter.

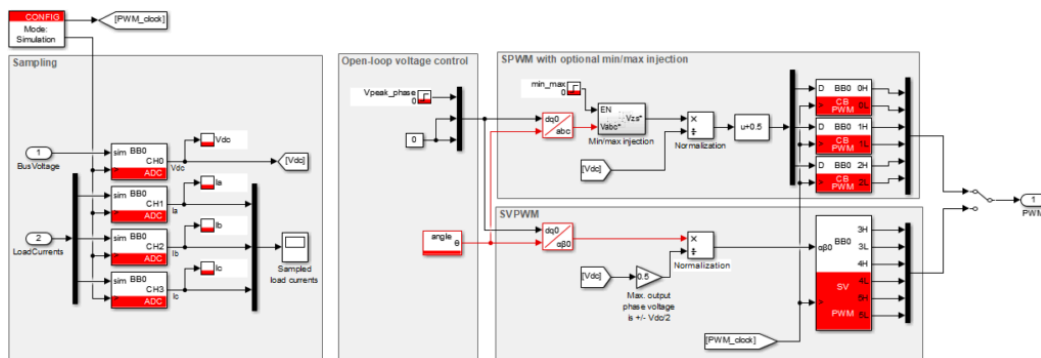[Download SVPWM vs SPWM control model](#)



Overview of the open-loop voltage control in Simulink with SVPWM or SPWM

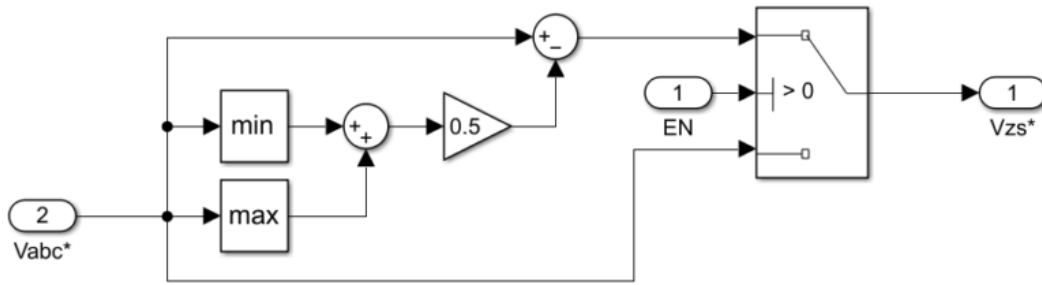The implementation of SVPWM with [Simulink](#) and the [ACG SDK](#) can be found in the [space vector modulation \(SVM\) note](#). Similarly, the details on the SPWM implementation can be found in the [three-phase inverter](#) note. Finally, the min/max injection for a carrier-based PWM is illustrated in the figure below.




Min/max injection for a carrier-based PWM

SVPWM and SPWM waveforms

During the experiments, the two-level converter was connected to a balanced three-phase RL load, under the following conditions:

- DC bus voltage: 100 V
- Control frequency and sampling: 20 kHz
- Sampling phase: 0.5
- Load resistance: 8.5 Ω
- Load inductance: 2.5 mH

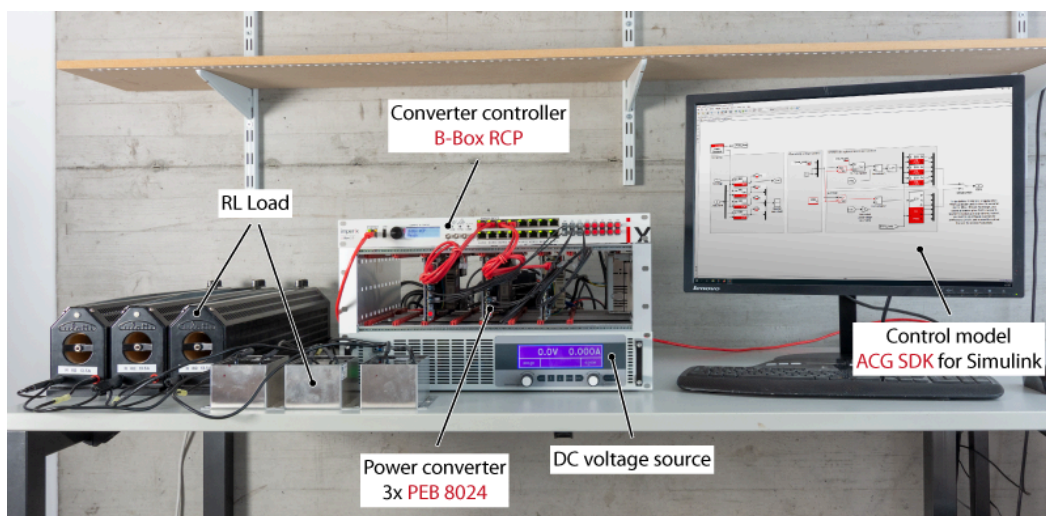
The experimental setup is presented in the picture below. The power converter is built from 3x [PEB 8024 phase-leg modules](#) and is controlled by a [B-Box RCP prototyping controller](#). The control software is implemented graphically using the [ACG SDK library for Simulink](#).



Experimental setup


The goal is to observe whether the line-to-line voltages are distorted or not, depending on the modulation scheme in use. Since the output line-to-line voltages of the converter are switched, it would require heavy filtering to extract sinusoidal waveforms. Instead, the line-to-line voltages can be observed indirectly through the load currents, since they are filtered by inductors. Then, in order to evaluate the impact of the modulation scheme, the modulation index is toggled between $m = 0.5$ and $m = 1.15$ each 60 ms.

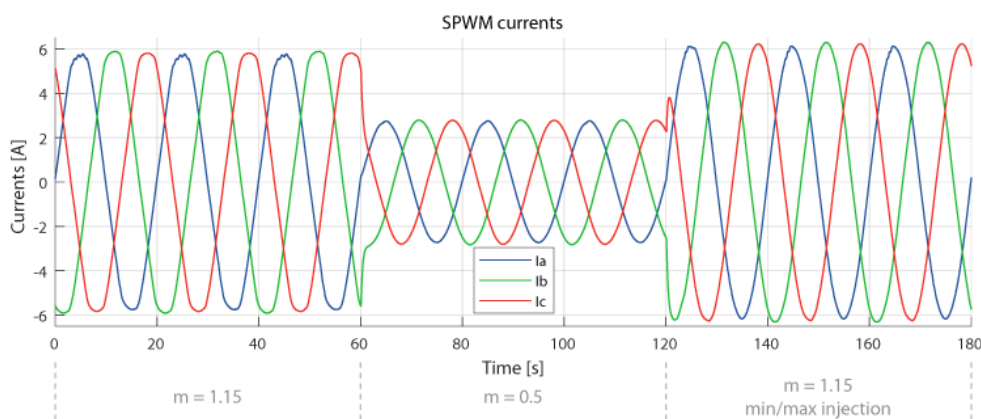When the modulation index is $m = 1.15$, the SPWM technique is in its overmodulation region. As a result, the output currents are flattened at their maximum, as shown in the figure below between $t = 0\text{ ms}$ and $t = 60\text{ ms}$. However, the currents are undistorted if the SPWM is used in combination with a min/max injection, as observed after $t = 120\text{ ms}$.




Experimental results of the SPWM modulation with or without min/max injection

The absence of distortion at $m = 1.15$ with min/max injection – or SVPWM, since the methods are equivalent – is easier to observe by superimposing the experimental currents obtained with SPWM and SVPWM, as shown below. For $m = 0.5$ though, the output voltages are within the capabilities of the DC bus with both modulation techniques, and the currents are identical regardless of the zero-sequence injection.

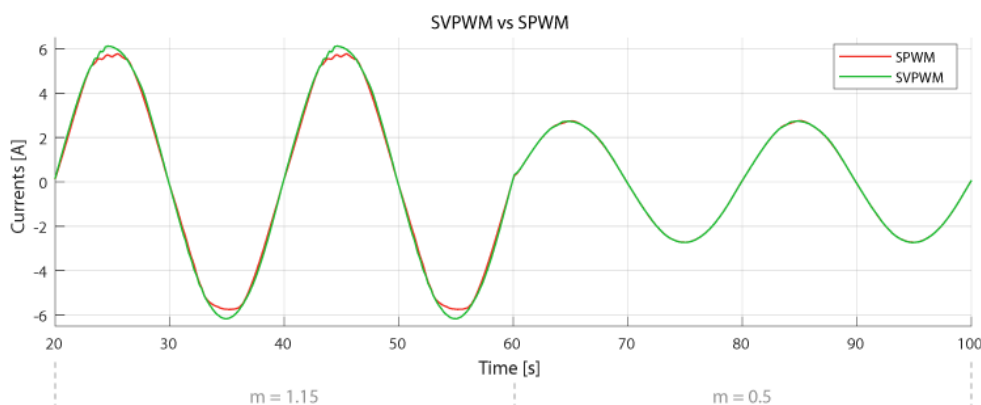


Experimental results illustrating the absence of distortion with SVPWM at $m = 1.15$, when compared to SPWM

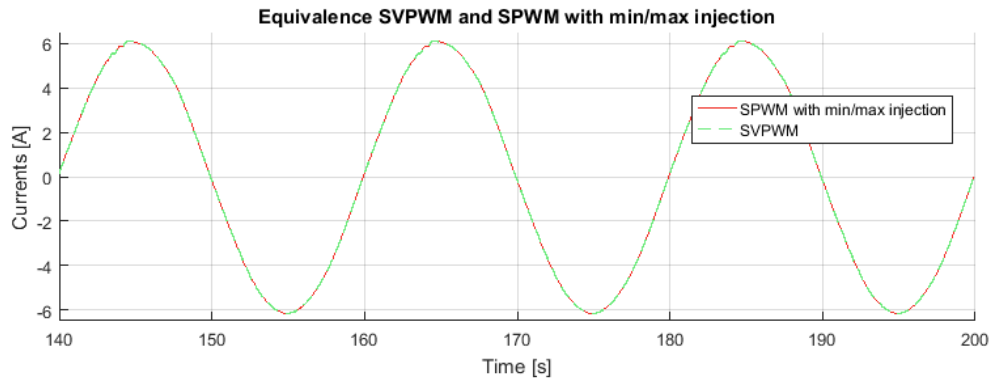The equivalence between SVPWM and SPWM with min/max injection was also verified experimentally, by using both methods with $m = 1.15$ and superimposing the measured currents, as shown below.




Experimental results illustrating the equivalence between SVPWM and SPWM with min/max injection

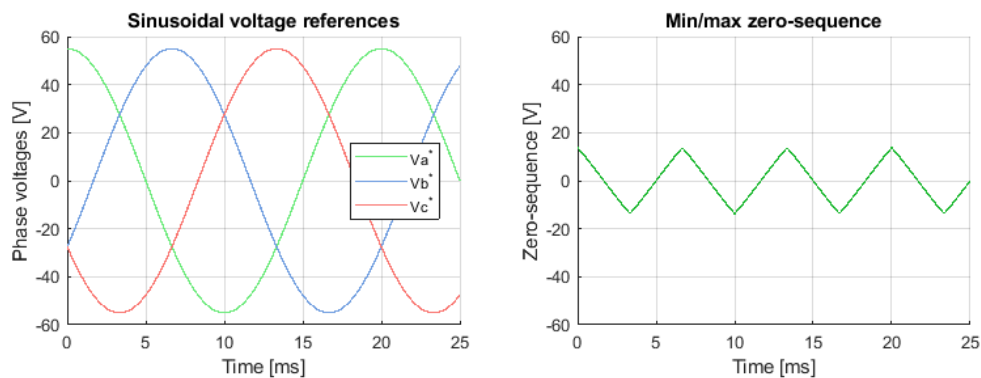While the voltage waveforms are challenging to measure experimentally (switched waveforms), their references can be observed directly from the control. The figure below illustrates side-by-side the sinusoidal voltage references and the corresponding min/max zero-sequence, with its characteristic triangular shape [1].



Min/max zero-sequence resulting from sinusoidal references (from simulation)

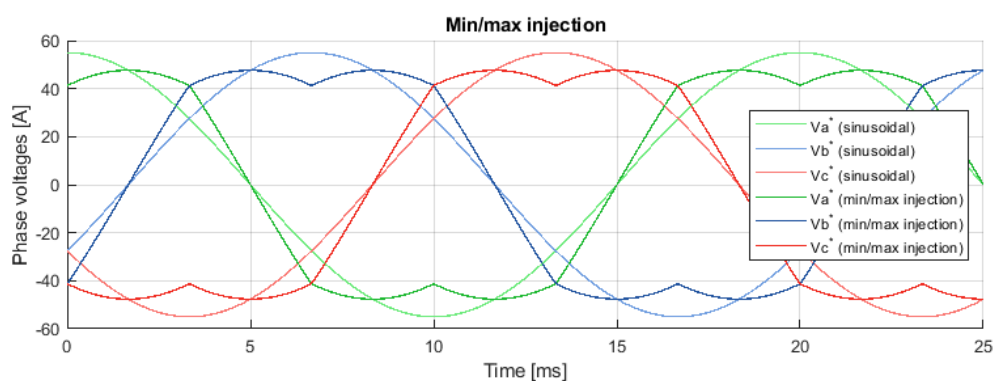By subtracting the zero-sequence from the sinusoidal waveforms, one can obtain the saddle-shaped voltage references from SVPWM.



Effect of the min/max injection on the phase voltage references (from simulation)

Academic references

[1] Slobodan N. Vukosavic, "Grid-Side Converters Control and Design", Springer, 2018, ISBN: 978-3-030-10346-0